

NAME: SOLUTIONS

Electronics Problems Involving Integration

Dawson College

Course Code: 201-NYA-05 S07

Date: May 2010

Instructor: E. Richer

17 p765

The electric current in a microprocessor circuit is $0.230 \mu\text{A}$. How many coulombs pass a given point in the circuit in 1.50 ms ?

$$i = 2.3 \times 10^{-7} \text{ A}$$

$$t = 0.0015 \text{ s}$$

$$q = \int i \, dt$$

$$= \int 2.3 \times 10^{-7} \, dt$$

$$= 2.3 \times 10^{-7} t$$

ASSUMING INITIAL CHARGE IS 0

$$q = (2.3 \times 10^{-7})(0.0015)$$

$$= \boxed{3.45 \times 10^{-10} \text{ C}}$$

19 p765

In an amplifier circuit, the current i (in A) changes with time t (in s) according to $i = 0.06t\sqrt{1+t^2}$. If 0.015 C of charge has passed a point in the circuit at $t = 0$, find the total charge to have passed the point at $t = 0.25$ s.

$$q = \int 0.06t \sqrt{1+t^2} dt$$
$$= \int 0.03 U^{1/2} du \quad \begin{array}{l} U = 1+t^2 \\ du = 2t dt \end{array}$$

$$q = 0.02 U^{3/2} + C_1$$

$$q = 0.02 (1+t^2)^{3/2} + C_1$$

$$\text{At } t=0, \quad q = 0.015$$

$$0.015 = 0.02(1)^{3/2} + C_1 \Rightarrow C_1 = -0.005$$

$$q = 0.02(1+t^2)^{3/2} - 0.005$$

At $t = 0.25$

$$q = 0.017 \text{ C}$$

20 p765

The current i (in μA) in a DVD player circuit is given by $i = 6.0 - 0.5t$, where t is the time in μs and $0 \leq t \leq 30\mu\text{s}$. If $q_0 = 0$ C, for what value of t is $q = 0$ C?

$$q = \int 6 - 0.5t dt$$

$$q = 6t - 0.25t^2 + C_1$$

$$0 = C_1$$

$$q = 6t - 0.25t^2$$

$$0 = 6t \left(1 - \frac{1}{24}t\right)$$

$$t=0 \quad \text{OR} \quad t = 24 \mu\text{s}$$

21 p765

The voltage across a $2.5 \mu\text{F}$ capacitor in a copying machine is zero. What is the voltage after 12 ms if a current of 25 mA charges the capacitor?

$$V_c = \frac{1}{C} \int i dt$$

$$= \frac{1}{2.5 \times 10^{-6}} \int 0.025 dt$$

$$V_c = \frac{1}{2.5} (10^6) (0.025t)$$

NO CONSTANT
b/c INITIAL VOLTAGE
is 0

at $t = 0.012 \text{ s}$

$$V_c = \frac{10^6}{2.5} (0.025)(0.012)$$

$$= \boxed{120 \text{ V}}$$

22 p765

The voltage across an 8.5 nF capacitor in an FM receiver circuit is zero. Find the voltage after $2.00 \mu\text{s}$ if a current (in mA) $i = 0.042t$ charges the capacitor.

$$V_c = \frac{1}{8.5 \times 10^{-9}} \int 0.042t \cdot 10^{-3} dt$$

$$= \frac{10^6}{8.5} (0.021t^2)$$

At $t = 2 \times 10^{-6} \text{ s}$

$$V_c = \boxed{9.88 \text{ nV}}$$

23 p765

The voltage across a $3.75 \mu\text{F}$ capacitor in a television circuit is 4.50 mV . Find the voltage after 0.565 ms if a current (in μA) $i = \sqrt[3]{1+6t}$ further charges the capacitor.

$$V_c = \frac{1}{3.75 \times 10^{-6}} \int (1+6t)^{\frac{1}{3}} \cdot 10^{-6} dt$$

$$= \frac{1}{3.75} \int (1+6t)^{\frac{1}{3}} dt$$

$$= \frac{1}{3.75} \left(\frac{1}{8} (1+6t)^{\frac{4}{3}} \right) + C_1$$

$$V_c = \frac{1}{30} (1+6t)^{\frac{4}{3}} + C_1$$

At $t=0$ $V_c = 0.0045$

$$0.0045 = \frac{1}{30} + C_1 \quad C_1 = -0.028833$$

$$V_c = \frac{1}{30} (1+6t)^{\frac{4}{3}} - 0.028833$$

At $t = 0.000565 \text{ s}$

$$V_c = 0.00465 \text{ V}$$

24 p765

A current $i = \frac{t}{\sqrt{t^2+1}}$ (in A) is sent through an electric dryer circuit containing a previously uncharged $2.0 \mu\text{F}$ capacitor. How long does it take for the capacitor voltage to reach 120V ?

$t=0$ $V_c=0$

$$V_c = \frac{1}{2 \times 10^{-6}} \int \frac{t}{\sqrt{t^2+1}} dt$$

$$V_c = \frac{1}{2 \times 10^{-6}} \sqrt{t^2+1} + C_1$$

$$0 = \frac{1}{2 \times 10^{-6}} + C_1 \quad C_1 = -500000$$

$$V_c = (0.5)10^6 \sqrt{t^2+1} - 500000$$

At $t=?$ does $V_c = 120\text{V}$?

$$120 = 0.5(10^6) \sqrt{t^2+1} - 500000$$

$$\sqrt{t^2+1} = 1.00024$$

$$t^2 = 0.00048$$

$$t = 0.0219$$

$$21.9 \text{ ms}$$